



Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

4-Bit-Relay-Adder

How does a Relay-CPU calculate?

Maximilian Noppel

July 18, 2020



Übersicht

Goals of the project	1 Goals of the project
How a relay works	2 How a relay works
Logic	3 Logic
Relay logic	4 Relay logic
Half/Full Adder	5 Half/Full Adder
Signed integers	6 Signed integers
Photos	7 Photos
Facts	8 Facts
Lessons learned	9 Lessons learned
Demo	10 Demo
What's next?	11 What's next?



Goals

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Preproject for EuroTwo
- Explainable binary calculation
- Design aspects
 - (indirect) LED indicators for everything and illumination in general
 - boardcolor
 - haptics, feeling



Goals

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Mechanical aspects
 - connectors, mounting, screws
 - powersupply
 - switches
- Electronical aspects
 - logic family



Inspiration

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

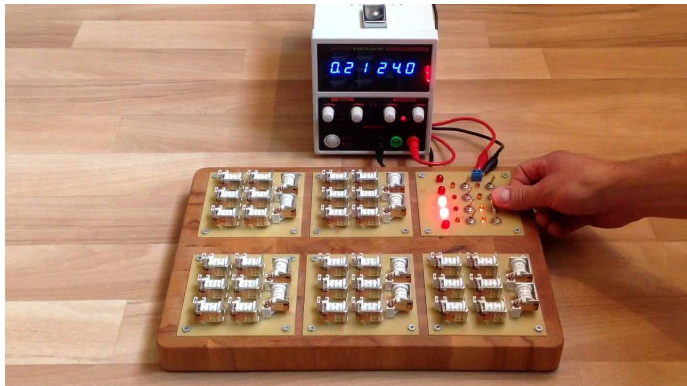



Mein Ergebnis

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?





Übersicht

Goals of the project

1 Goals of the project

How a relay works

2 How a relay works

Logic

3 Logic

Relay logic

4 Relay logic

Half/Full Adder

5 Half/Full Adder

Signed integers

6 Signed integers

Photos

7 Photos

Facts

8 Facts

Lessons learned

9 Lessons learned

Demo

10 Demo

What's next?

11 What's next?



Relays

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

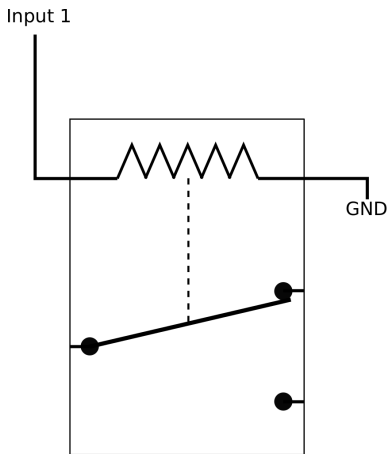



Relays

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

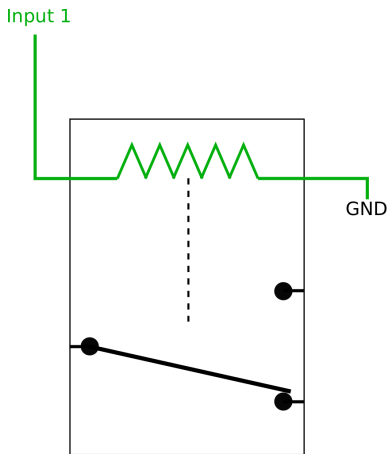



Übersicht

Goals of the project

1 Goals of the project

How a relay works

2 How a relay works

Logic

3 Logic

Relay logic

4 Relay logic

Half/Full Adder

5 Half/Full Adder

Signed integers

6 Signed integers

Photos

7 Photos

Facts

8 Facts

Lessons learned

9 Lessons learned

Demo

10 Demo

What's next?

11 What's next?



Binary

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Working with 0,1
- Logic gates
 - AND, OR, XOR, NOT, NOR, NAND
- Combining to building blocks
 - Half/Full Adder, Registers, Counters, Multiplexer, Decoder, ...



Binary

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

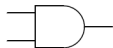

AND

A	B	Output
0	0	0
0	1	0
1	0	0
1	1	1



NAND

A	B	Output
0	0	1
0	1	1
1	0	1
1	1	0



OR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	1



NOR

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	0



XOR

A	B	Output
0	0	0
0	1	1
1	0	1
1	1	0



XNOR

A	B	Output
0	0	1
0	1	0
1	0	0
1	1	1



Übersicht

Goals of the project	1	Goals of the project
How a relay works	2	How a relay works
Logic	3	Logic
Relay logic	4	Relay logic
Half/Full Adder	5	Half/Full Adder
Signed integers	6	Signed integers
Photos	7	Photos
Facts	8	Facts
Lessons learned	9	Lessons learned
Demo	10	Demo
What's next?	11	What's next?



Relay logic

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

0	1
floating	+5V
GND	+5V



AND Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

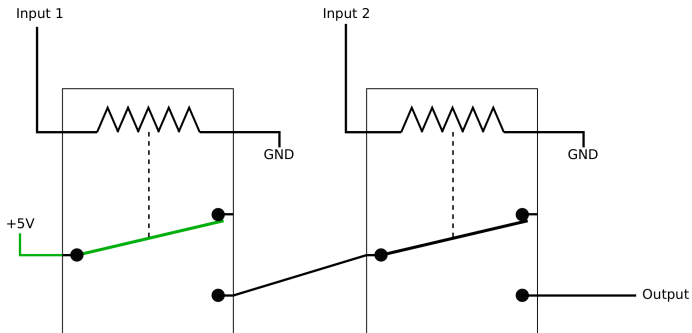



AND Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

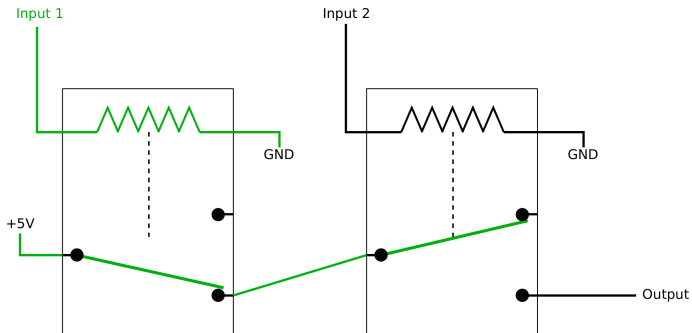



AND Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

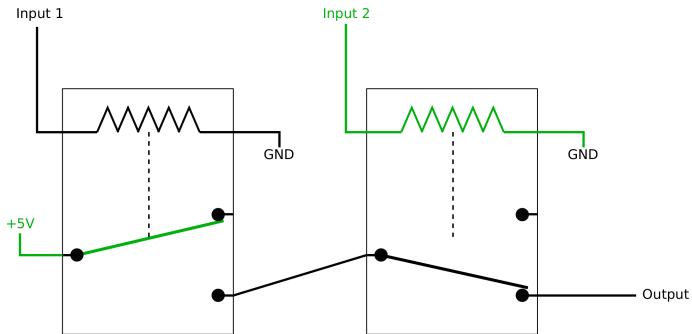



AND Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

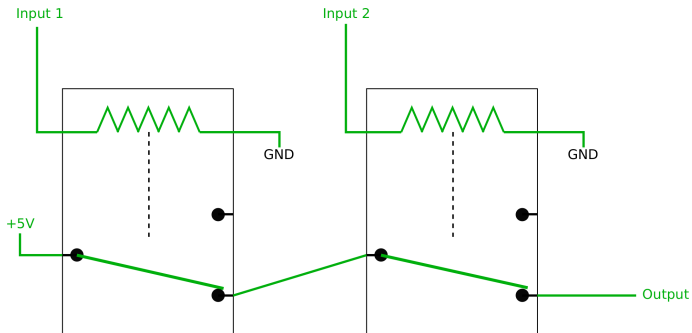



XOR Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

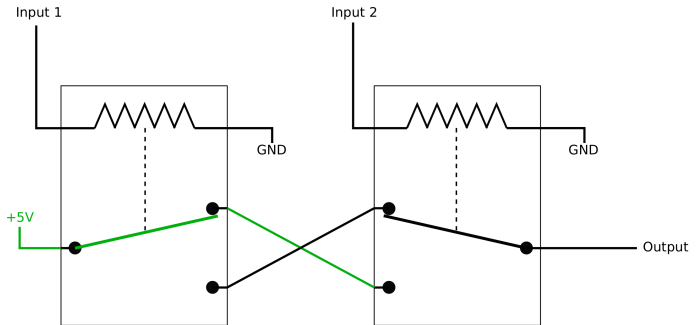



XOR Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

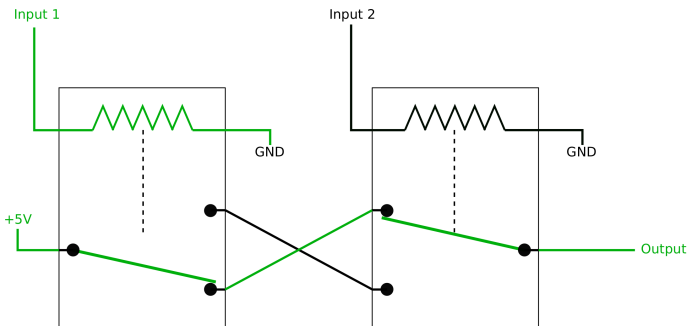



XOR Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

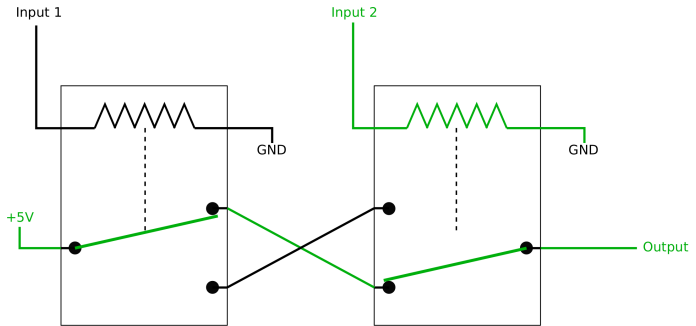



XOR Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

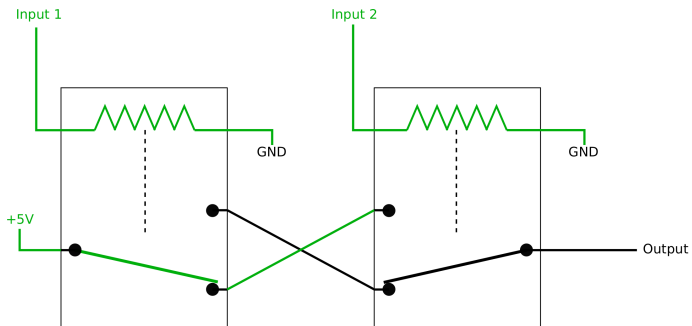



OR Gate

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

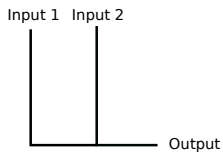



Übersicht

Goals of the project	1	Goals of the project
How a relay works	2	How a relay works
Logic	3	Logic
Relay logic	4	Relay logic
Half/Full Adder	5	Half/Full Adder
Signed integers	6	Signed integers
Photos	7	Photos
Facts	8	Facts
Lessons learned	9	Lessons learned
Demo	10	Demo
What's next?	11	What's next?



Half Adder

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

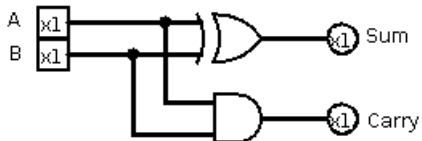

A	B	Carry	Sum	CarrySum
0	0	0	0	00
0	1	0	1	01
0	0	0	1	01
1	1	1	0	10



Full Adder

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

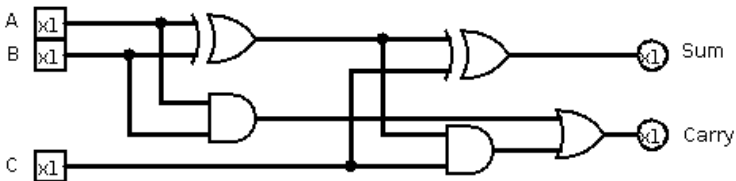


A	B	C	Carry	Sum	CarrySum
0	0	0	0	0	00
0	0	1	0	1	01
0	1	0	0	1	01
0	1	1	1	0	10
1	0	0	0	1	01
1	0	1	1	0	10
1	1	0	1	0	10
1	1	1	1	1	11



1 Bit Full Adder in Relays

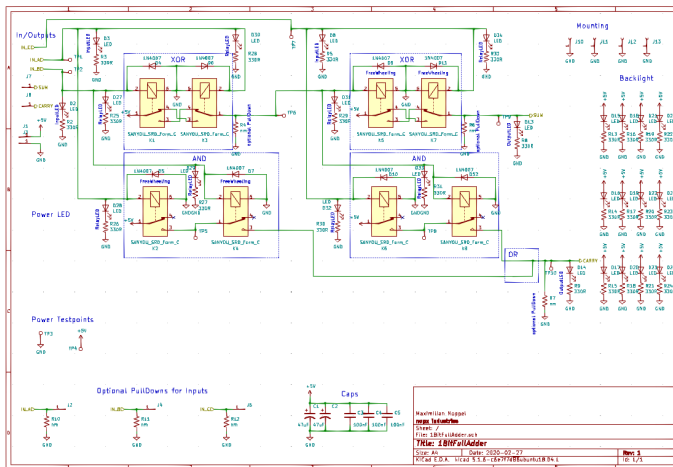- Goals of the project
- How a relay works
- Logic
- Relay logic
- Half/Full Adder
- Signed integers
- Photos
- Facts
- Lessons learned
- Demo
- What's next?





4 Bit Adder

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

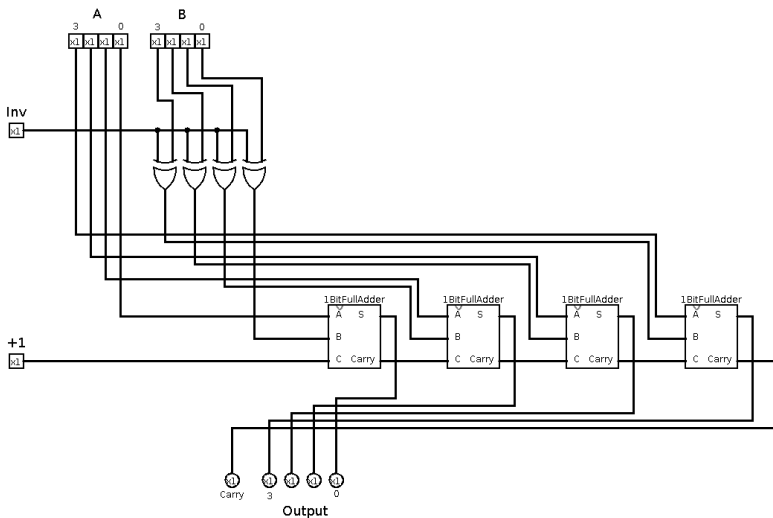



Übersicht

Goals of the project	1	Goals of the project
How a relay works	2	How a relay works
Logic	3	Logic
Relay logic	4	Relay logic
Half/Full Adder	5	Half/Full Adder
Signed integers	6	Signed integers
Photos	7	Photos
Facts	8	Facts
Lessons learned	9	Lessons learned
Demo	10	Demo
What's next?	11	What's next?



Unsigned integers

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

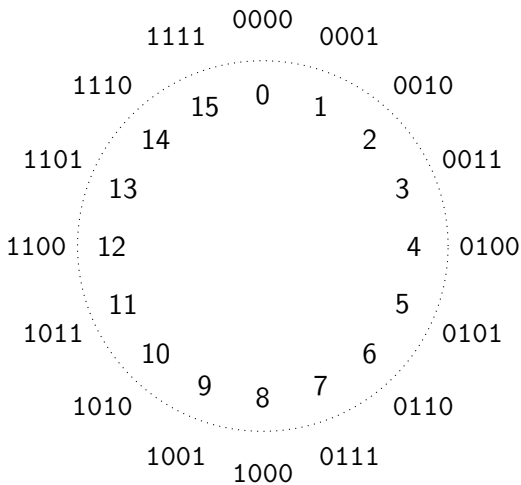



Two's complement

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

0010 | 2

|

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?



Two's complement

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

0010		2		
1101		one's complement of 2		<i>invert</i>



Two's complement

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

0010		2		
1101		one's complement of 2		<i>invert</i>
1110		-2 (two's complement of 2)		+1



Two's complement

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

0010		2		
1101		one's complement of 2		<i>invert</i>
1110		-2 (two's complement of 2)		+1
0001		one's complement of -2		<i>invert</i>



Two's complement

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

0010		2		
1101		one's complement of 2		<i>invert</i>
1110		-2 (two's complement of 2)		+1
0001		one's complement of -2		<i>invert</i>
0010		2 (two's complement of -2)		+1



Signed integers

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

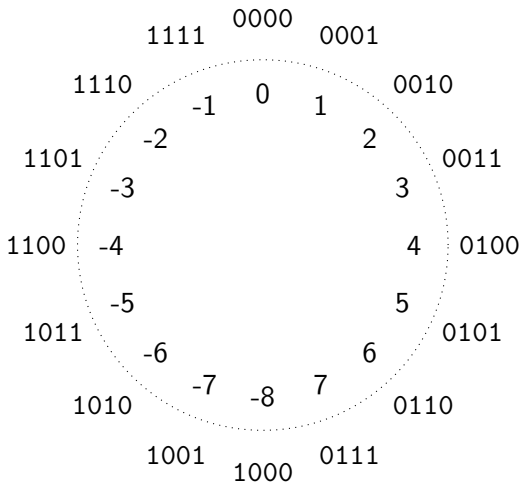



Solution to use signed integers

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Add controlled inverter
- Switch for C_0



4 Bit Adder

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

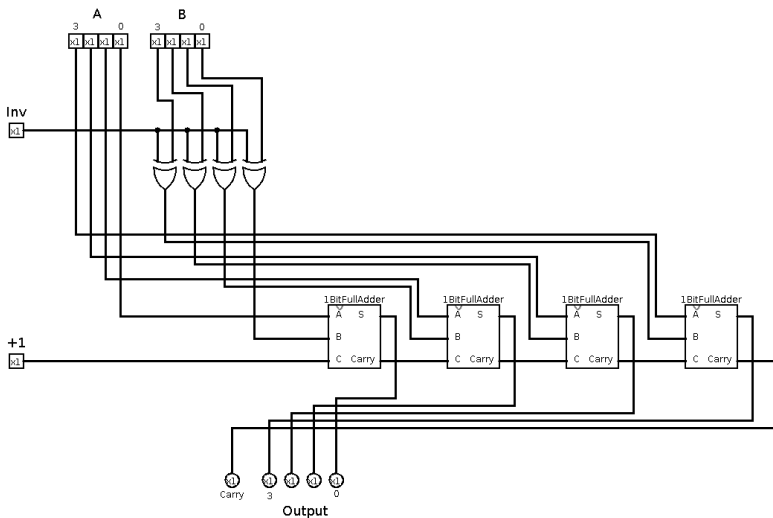



Übersicht

Goals of the project	1	Goals of the project
How a relay works	2	How a relay works
Logic	3	Logic
Relay logic	4	Relay logic
Half/Full Adder	5	Half/Full Adder
Signed integers	6	Signed integers
Photos	7	Photos
Facts	8	Facts
Lessons learned	9	Lessons learned
Demo	10	Demo
What's next?	11	What's next?



The finished Adder

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?





The backboard

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?





The lights

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

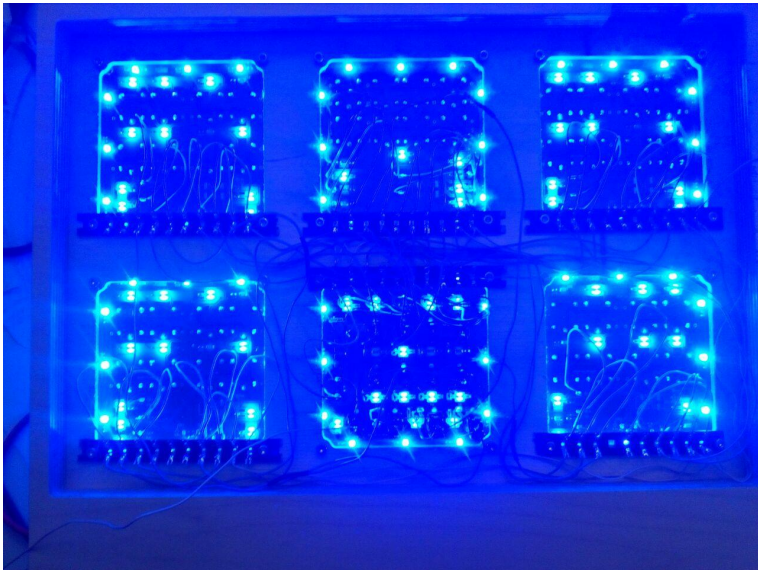



The wires

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

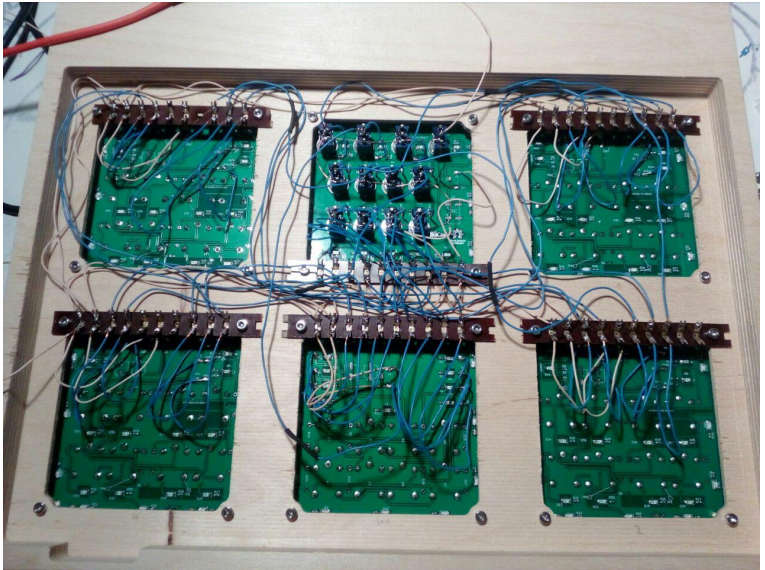



Übersicht

Goals of the project	1	Goals of the project
How a relay works	2	How a relay works
Logic	3	Logic
Relay logic	4	Relay logic
Half/Full Adder	5	Half/Full Adder
Signed integers	6	Signed integers
Photos	7	Photos
Facts	8	Facts
Lessons learned	9	Lessons learned
Demo	10	Demo
What's next?	11	What's next?



Facts!

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

Current:

- 90mA per Relay
- $\sim 2.6A$

Frequency:

- 10ms per Relay
- Targetfrequency of EuroTwo: 2 – 4Hz

Price:

- Don't ask!



Übersicht

Goals of the project	1	Goals of the project
How a relay works	2	How a relay works
Logic	3	Logic
Relay logic	4	Relay logic
Half/Full Adder	5	Half/Full Adder
Signed integers	6	Signed integers
Photos	7	Photos
Facts	8	Facts
Lessons learned	9	Lessons learned
Demo	10	Demo
What's next?	11	What's next?



Lessons learned

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Backlight illumination is not worth it
- (Data)wires on the front would help explaining how it works!
- LED Backillumination: Use Cu on the front!
- Use connectors for the switches



Lessons learned

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Use DPDT Relay for MUX, DEC and Registers
- Better labels for signed calculation! Or now labels at all.
- White PCBs are better!
- Do not solder every single wire → screws!



Übersicht

- | | | |
|----------------------|----|----------------------|
| Goals of the project | 1 | Goals of the project |
| How a relay works | 2 | How a relay works |
| Logic | 3 | Logic |
| Relay logic | 4 | Relay logic |
| Half/Full Adder | 5 | Half/Full Adder |
| Signed integers | 6 | Signed integers |
| Photos | 7 | Photos |
| Facts | 8 | Facts |
| Lessons learned | 9 | Lessons learned |
| Demo | 10 | Demo |
| What's next? | 11 | What's next? |



Demo

Goals of the
project

How a relay
works

Logic

Relay logic

Half/Full
Adder

Signed
integers

Photos

Facts

Lessons
learned

Demo

What's next?

Live demo!



Übersicht

- | | | |
|----------------------|----|----------------------|
| Goals of the project | 1 | Goals of the project |
| How a relay works | 2 | How a relay works |
| Logic | 3 | Logic |
| Relay logic | 4 | Relay logic |
| Half/Full Adder | 5 | Half/Full Adder |
| Signed integers | 6 | Signed integers |
| Photos | 7 | Photos |
| Facts | 8 | Facts |
| Lessons learned | 9 | Lessons learned |
| Demo | 10 | Demo |
| What's next? | 11 | What's next? |



Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

- Most of the PCB are planned and layouted. Just need to order.
- ControlUnit (CU) left
- Datawires on the front, connected via screws
- Powersupply on the back, through mountings
- No backlight illumination
- PWR LED on the back of each PCB
- Size: $5 \times 5 = 25$ PCBs



Euro Two

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?





EuroTwo

Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers


Photos

Facts

Lessons learned

Demo

What's next?

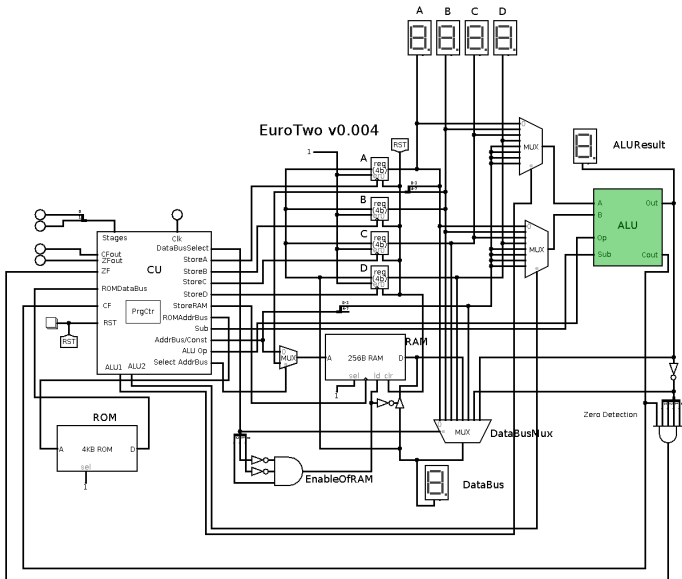



Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

Questions?

The beamer template is online!

`https://wiki.vspace.one/lib/exe/fetch.php?media=20180918_template_presentation.zip`



Goals of the project

How a relay works

Logic

Relay logic

Half/Full Adder

Signed integers

Photos

Facts

Lessons learned

Demo

What's next?

For all images and visualization:

- either the source is denoted on the slides or
- they are licenced under CC BY 4.0 by Maximilian Noppel
- [?]